

# Electric Energy Conversion

## 8. DC/AC converters – part 2

Vinícius Lacerda  
Electrical Engineering Department  
CITCEA-UPC




# Outline


- Multilevel inverters
- Simulation
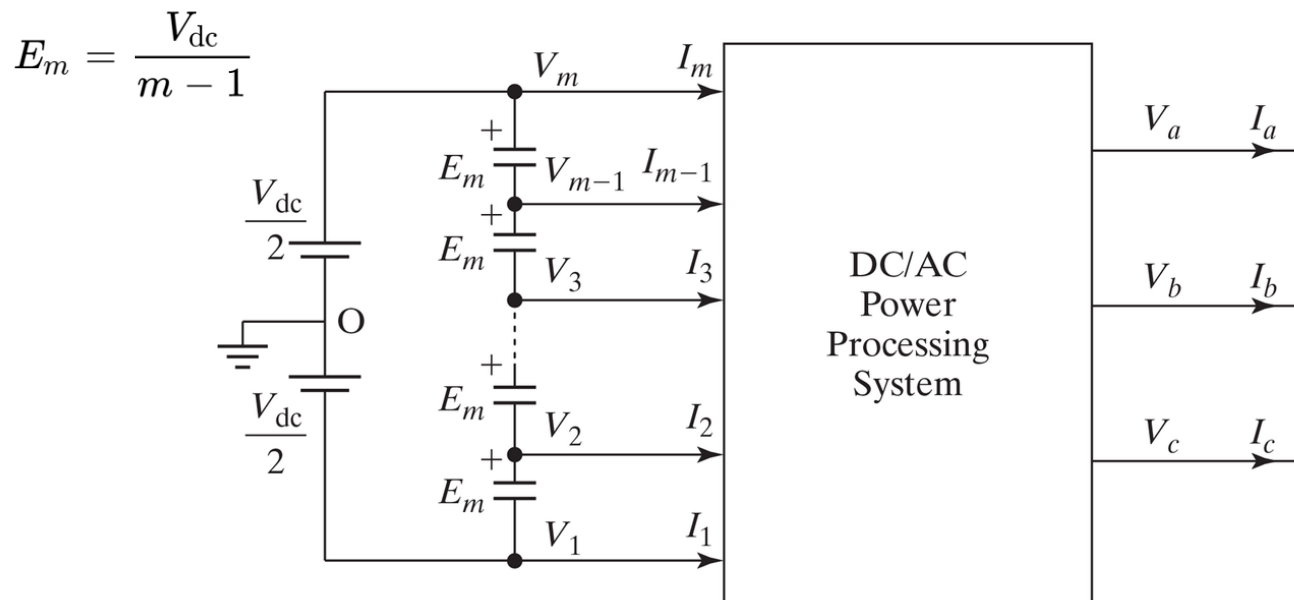
# Introduction

- Multilevel inverters have drawn much interest in the power industry, transportation and renewable energy.
- With multilevel inverters, it is easier to produce high-power, high-voltage inverters due to how device voltage stresses are controlled in the structure.
- With higher voltage levels, lower switching frequencies can be used, producing higher quality waveforms.



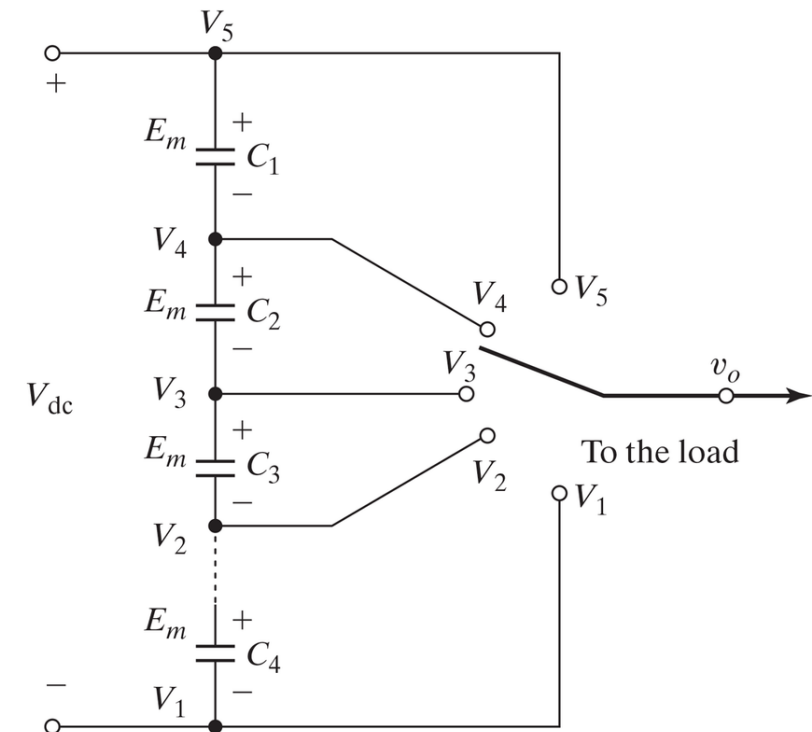(a) Three-phase multilevel power processing system




(b) Schematic of single pole of multilevel inverter


# Principle of operation – half-bridge

- The AC waveform is generated from the series connection of charged capacitors.

$$E_m = \frac{V_{dc}}{m - 1}$$

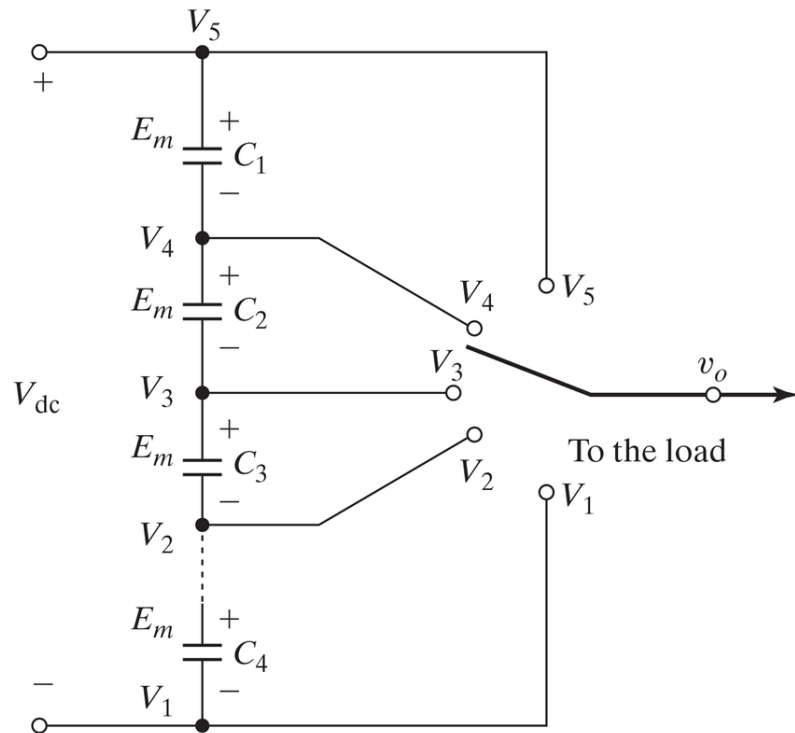


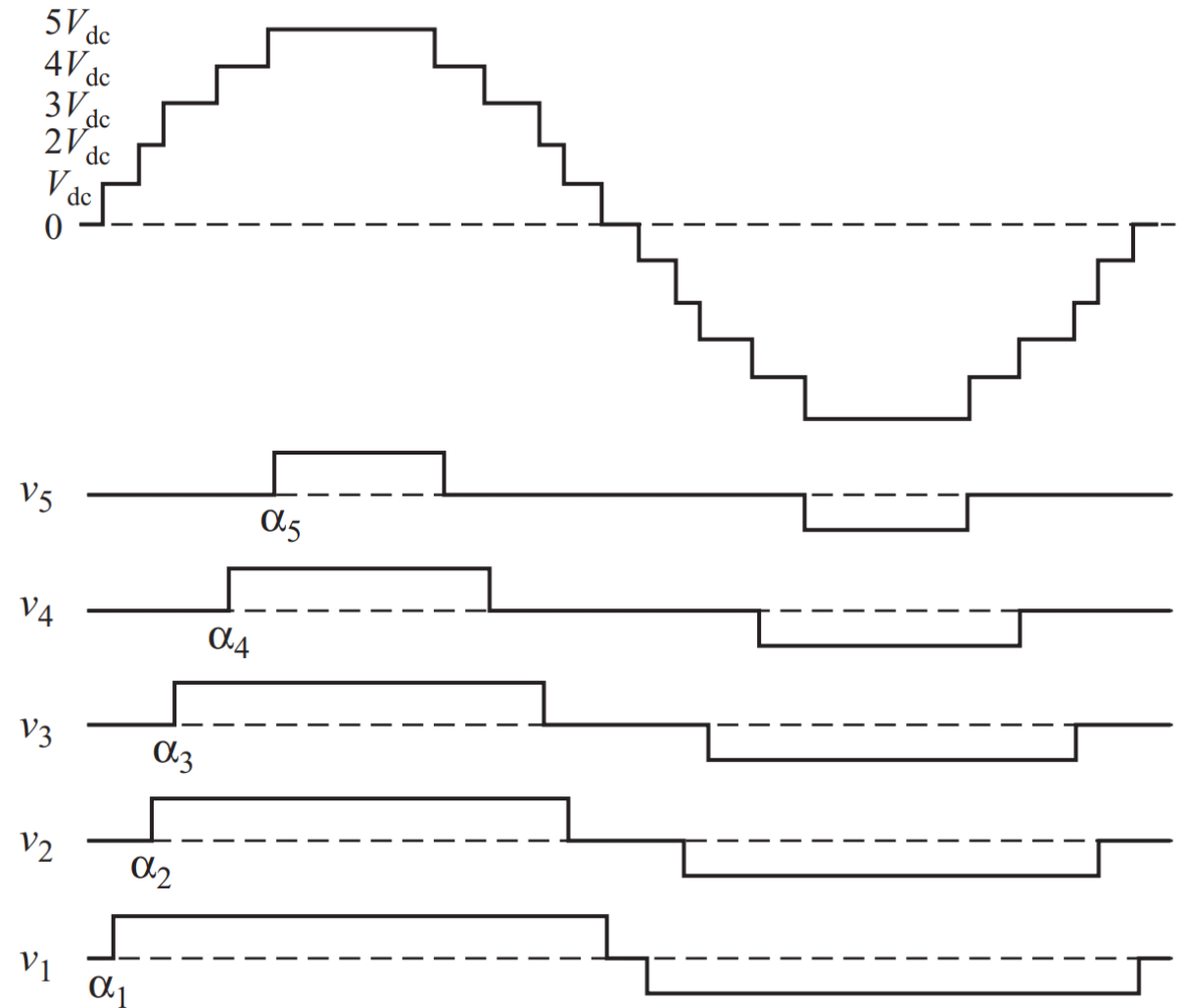
(b) Schematic of single pole of multilevel inverter



# Diode-clamped multilevel inverter

- The diode-clamped topology typically consists of  $(m-1)$  capacitors on the DC bus and produces  $m$  voltage levels. The switches are turned ON in the staircase.
- Although each switch is required to block a voltage level of  $V_{dc}/(m-1)$ , the clamped diodes need to have different reverse voltage blocking ratings.
- Excessive number of clamping diodes are required when the number of levels is high.
- Improved topologies were proposed.

Output $v_{a0}$	Switch State							
	$S_{a1}$	$S_{a2}$	$S_{a3}$	$S_{a4}$	$S'_{a1}$	$S'_{a2}$	$S'_{a3}$	$S'_{a4}$
$V_5 = V_{dc}$	1	1	1	1	0	0	0	0
$V_4 = 3V_{dc}/4$	0	1	1	1	1	0	0	0
$V_3 = V_{dc}/2$	0	0	1	1	1	1	0	0
$V_2 = V_{dc}/4$	0	0	0	1	1	1	1	0
$V_1 = 0$	0	0	0	0	1	1	1	1

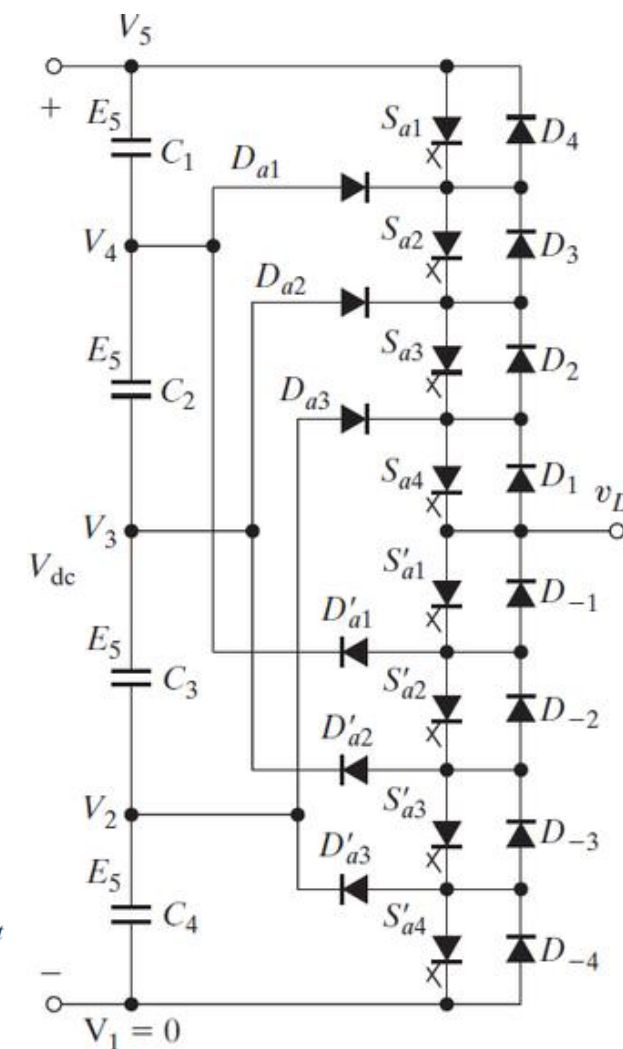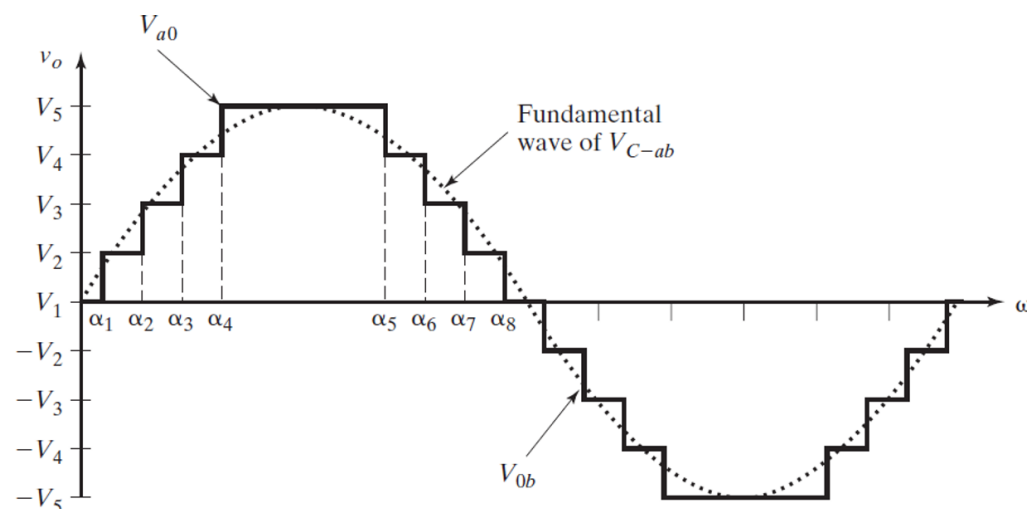


(a) One leg of a bridge

# Flying-Capacitors Multilevel Inverter


- The flying-capacitors topology consists on an inner loop of balancing capacitors to provide the required voltage steps.
- This topology requires  $(m-1) \times (m-2)/2$  capacitors, more than other topologies

Output $v_{a0}$	Switch State							
	$S_{a1}$	$S_{a2}$	$S_{a3}$	$S_{a4}$	$S'_{a4}$	$S'_{a3}$	$S'_{a2}$	$S'_{a1}$
$V_5 = V_{dc}$	1	1	1	1	0	0	0	0
$V_4 = 3V_{dc}/4$	1	1	1	0	1	0	0	0
$V_3 = V_{dc}/2$	1	1	0	0	1	1	0	0
$V_2 = V_{dc}/4$	1	0	0	0	1	1	1	0
$V_1 = 0$	0	0	0	0	1	1	1	1

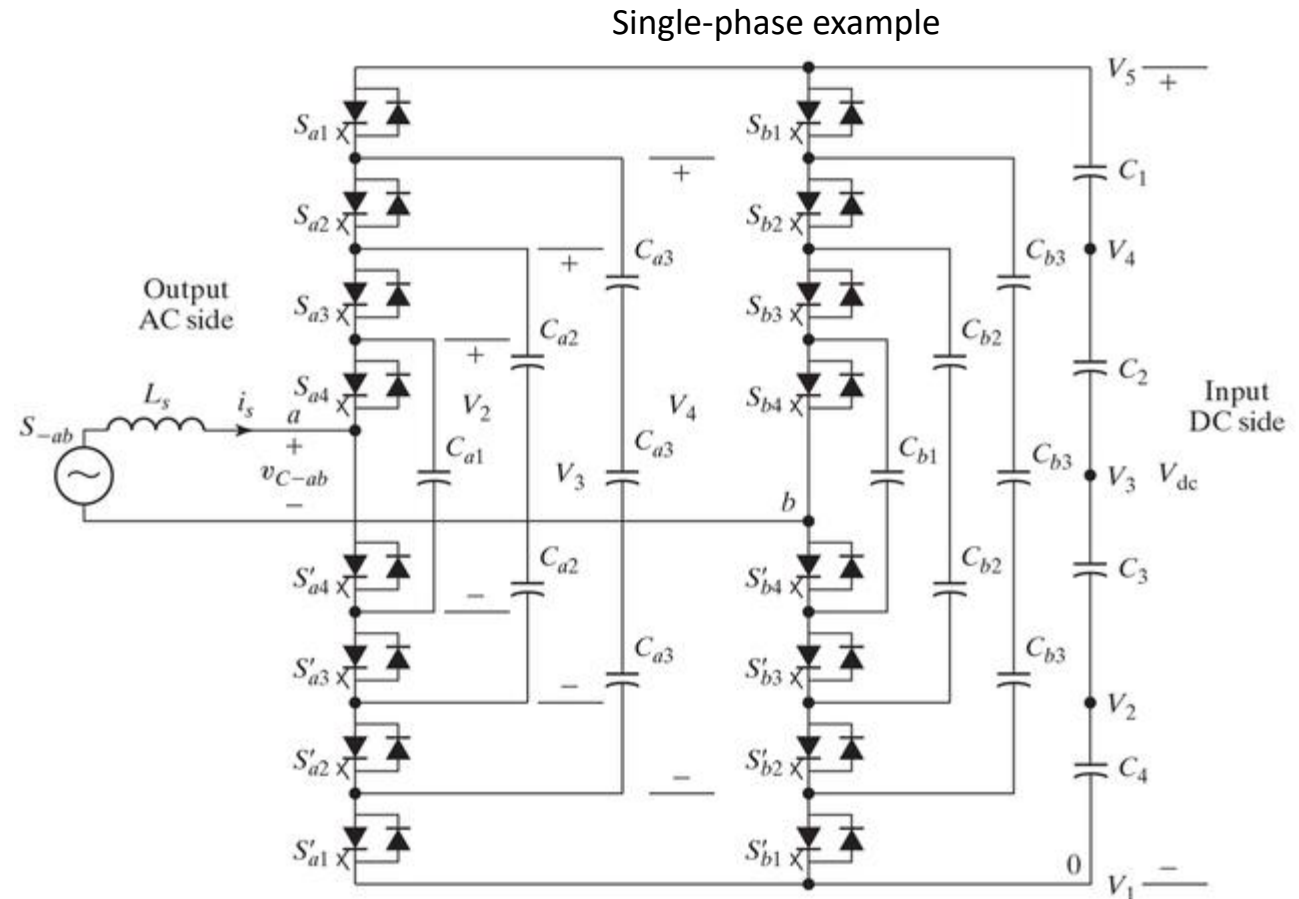


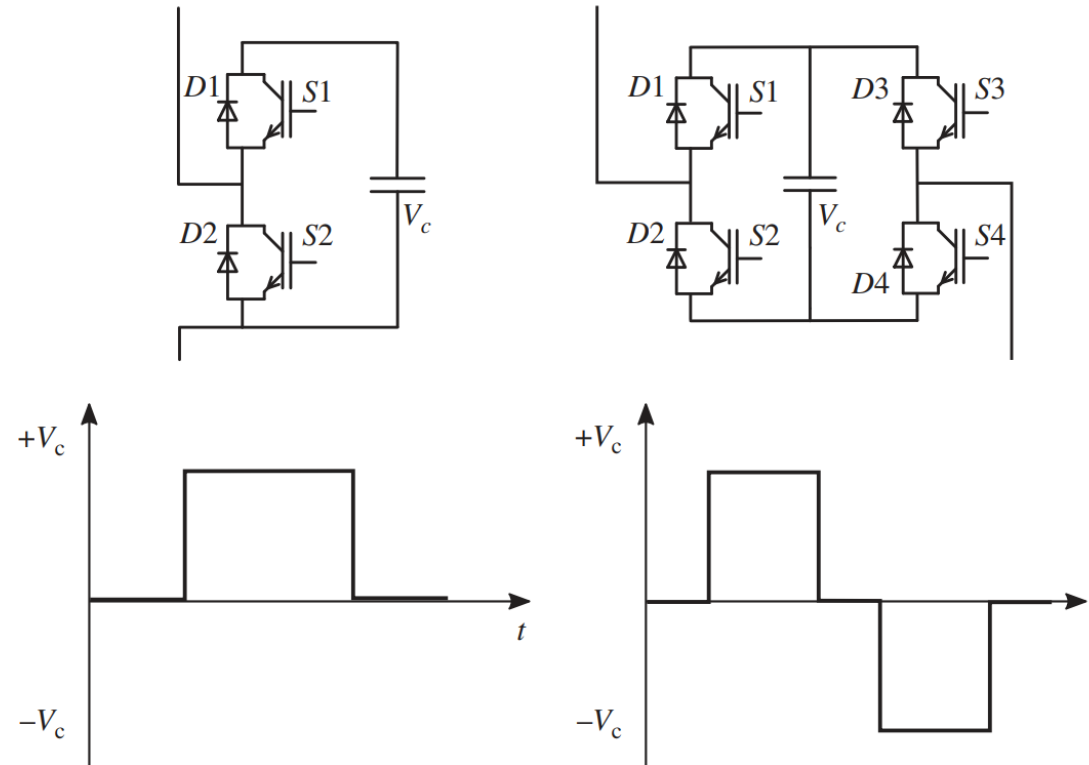
# Cascaded Multilevel Inverter

- The building blocks of cascaded multilevel converters are the switching submodules (also called cells).
- The submodules can be half-bridge or full-bridge. The half-bridge can generate 0 or  $+V_c$  and the full bridge can generate three voltage levels: 0,  $+V_c$ ,  $-V_c$ . When the switching function is 0 the submodule is bypassed. When it is 1 the submodule is inserted. The full bridge has two switching functions.



# Cascaded Multilevel Inverter

- Example with cascaded half-bridges

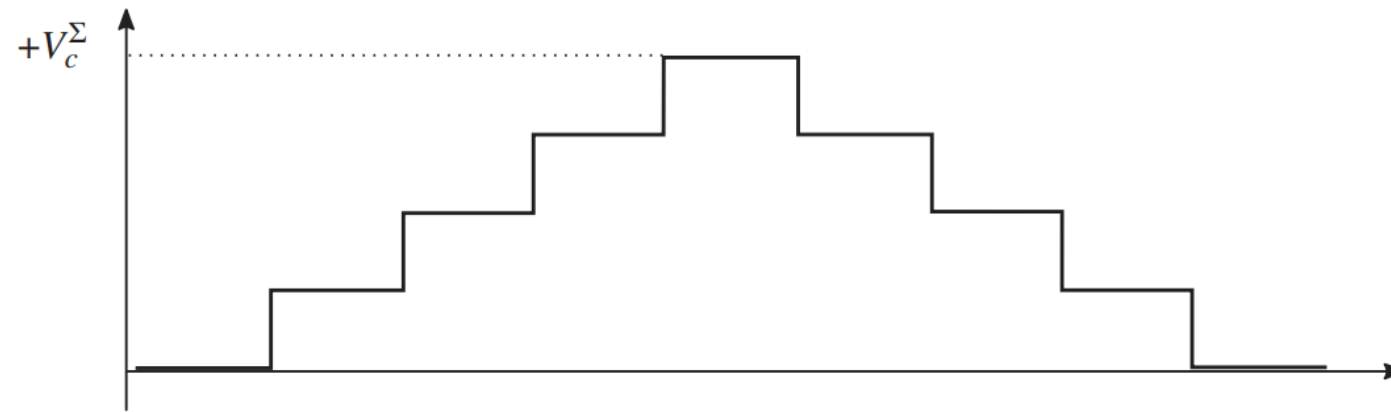
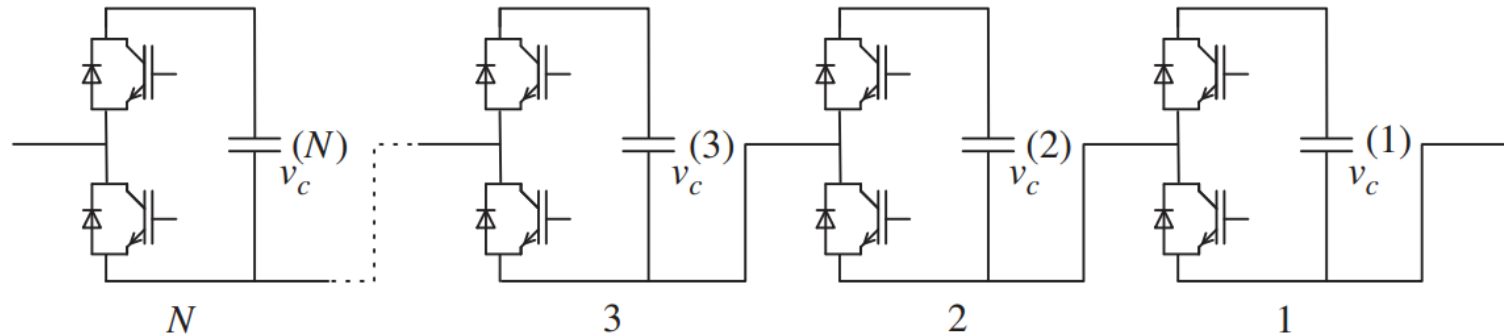


Half-bridge string and possible voltage levels



# Cascaded Multilevel Inverter



- Example with cascaded full-bridges

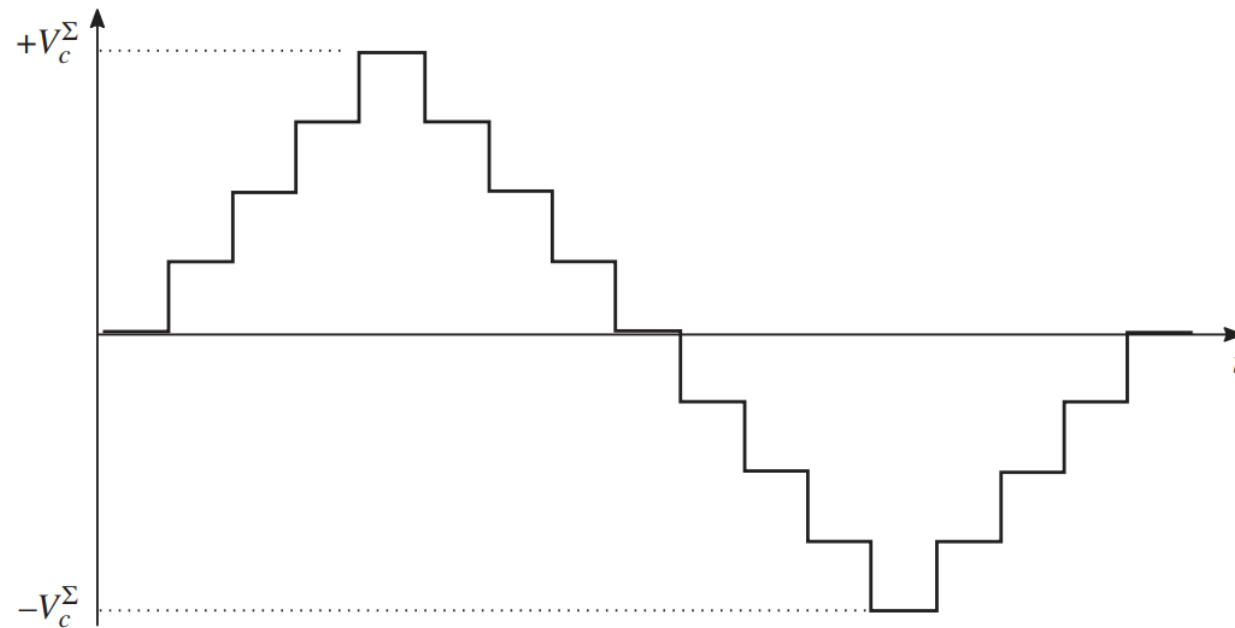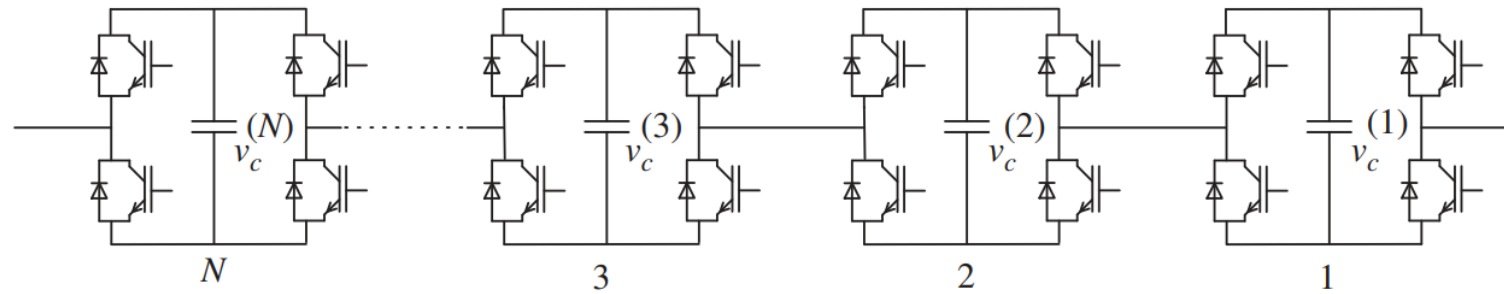

Full-bridge string and possible voltage levels

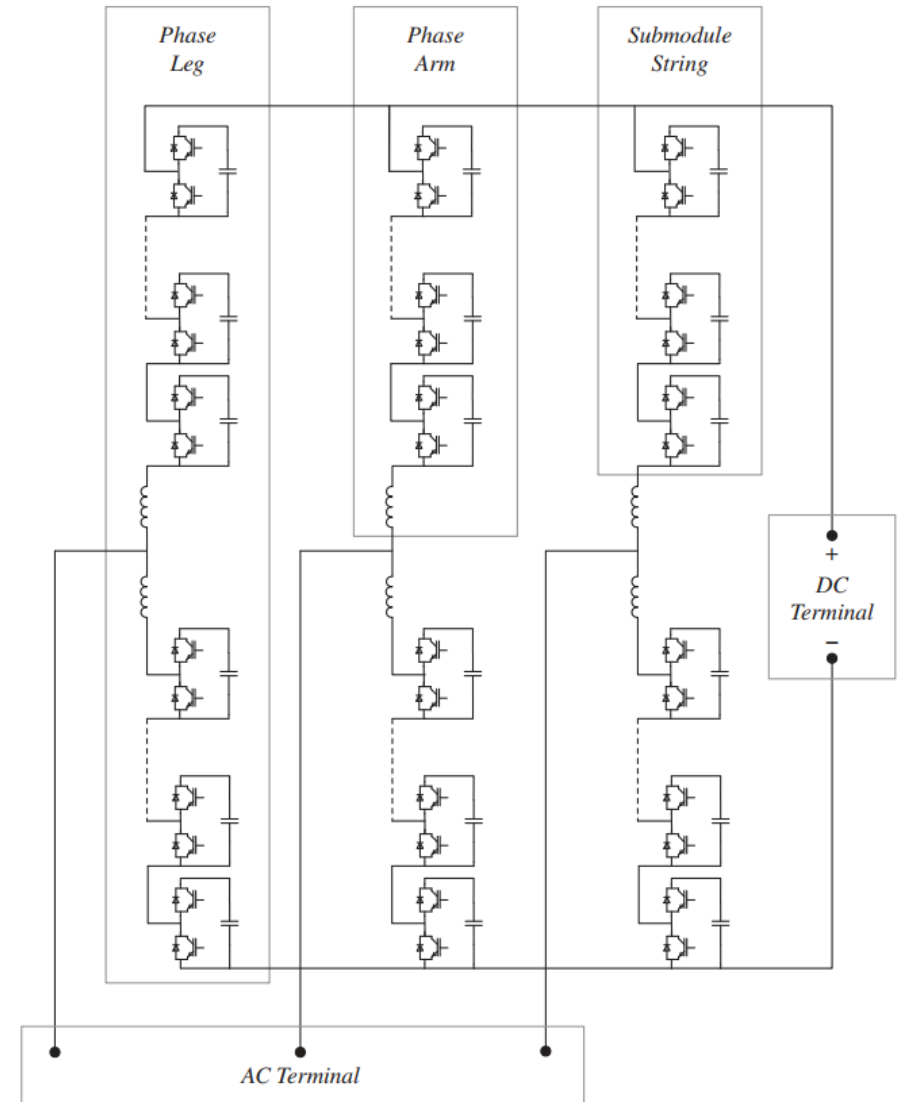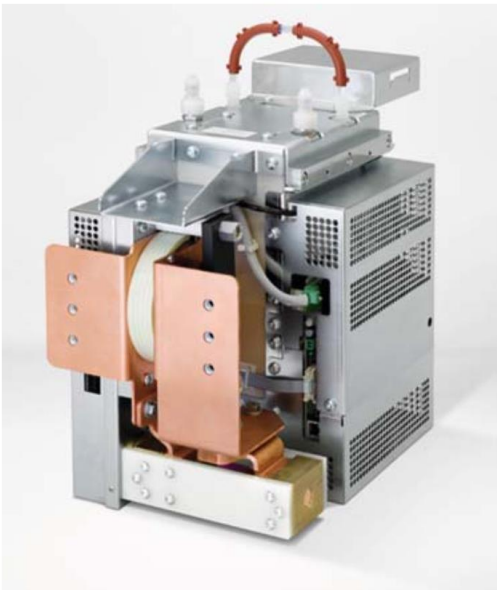
# Modular Multilevel Converter

- An AC voltage waveform can be produced either with half-bridges or full-bridges.
- In the star configuration the submodules are connected such that the midpoint of the string is connected to the grid,


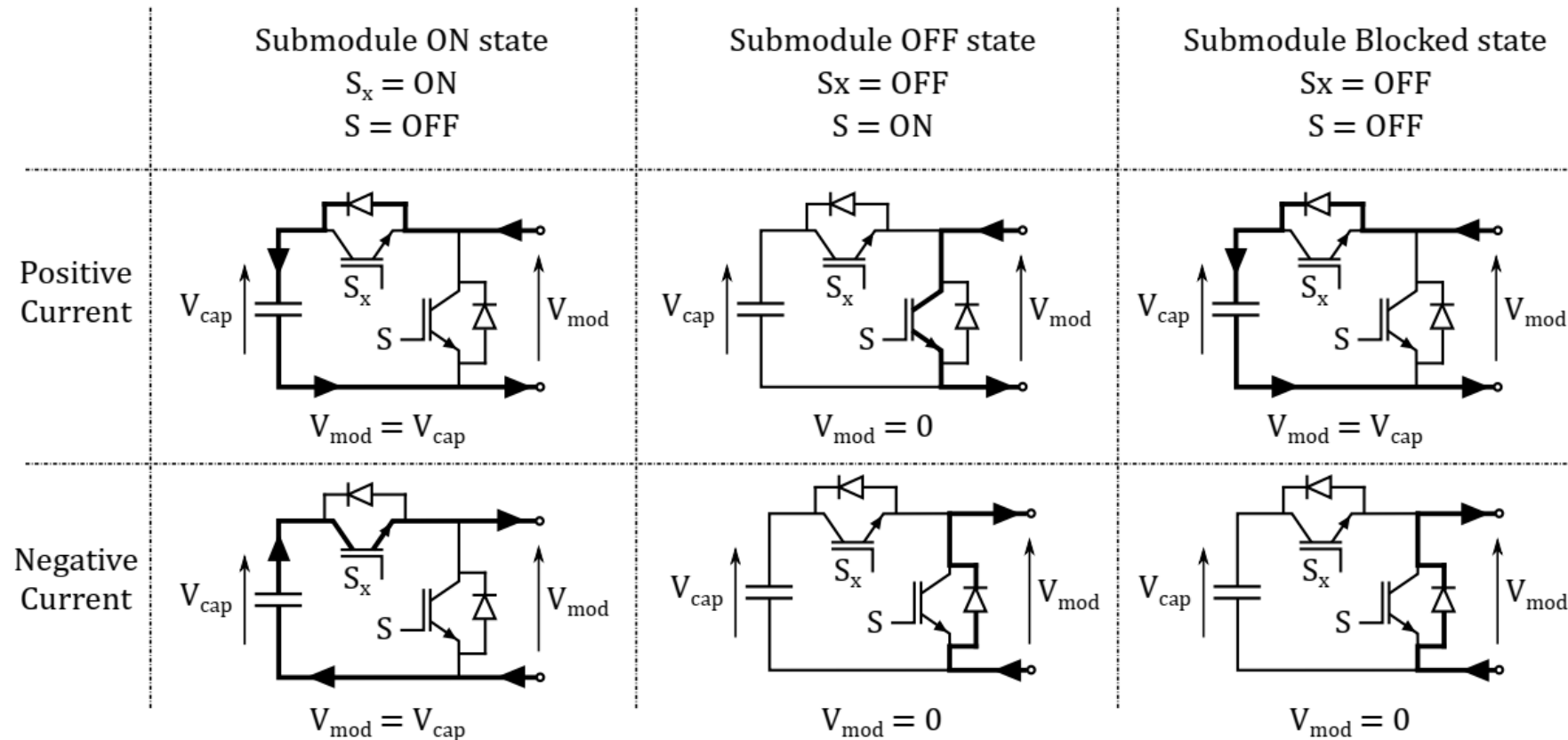
# Modular Multilevel Converter


- Depending on the sign of the current, the capacitors can charge or discharge. As a consequence, the energy across capacitors is not balanced. Thus, an energy balance algorithm is used to keep the capacitors evenly charged.




# Modular Multilevel Converter

- There are two main types of modulation for MMCs:

## Multilevel PWM

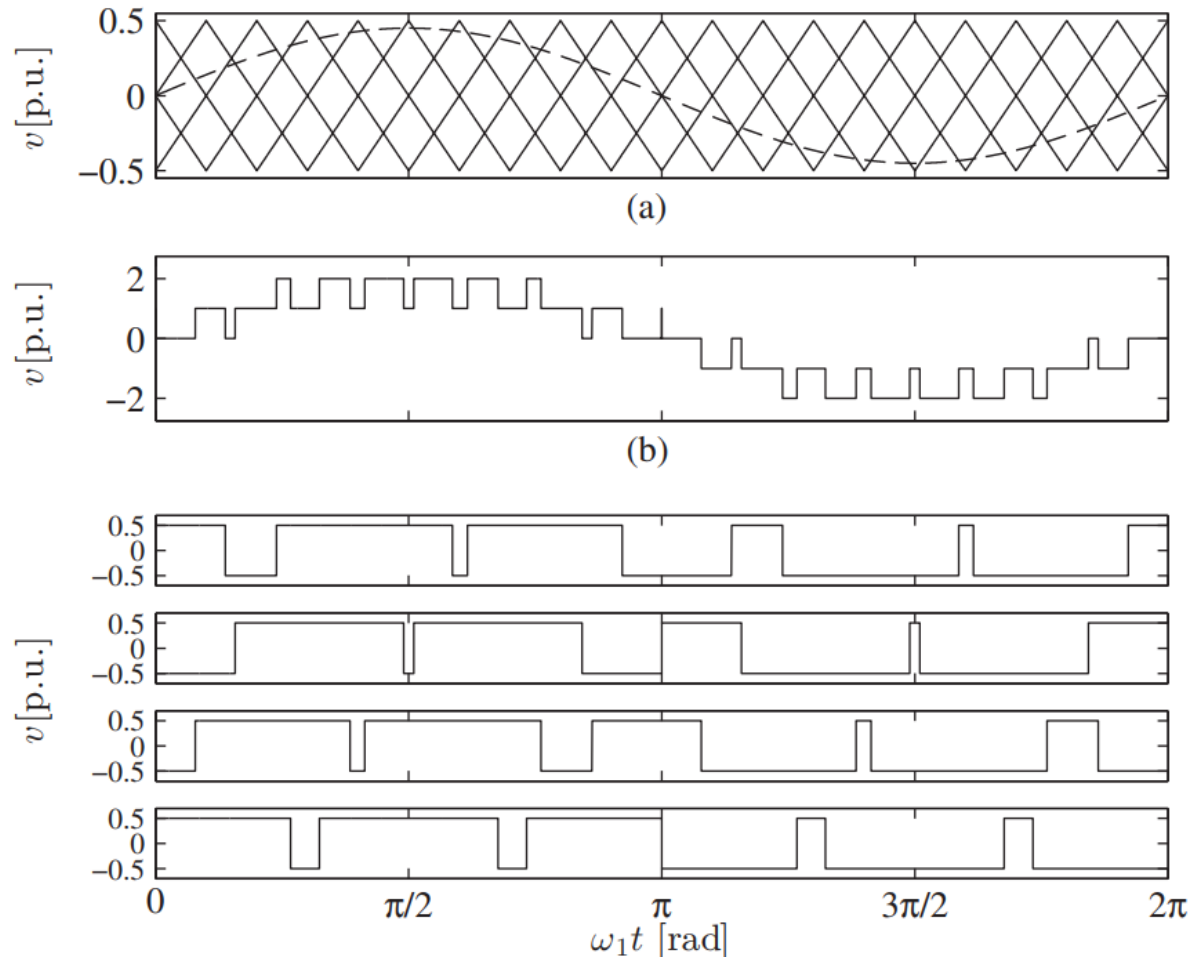

## Nearest-level modulation

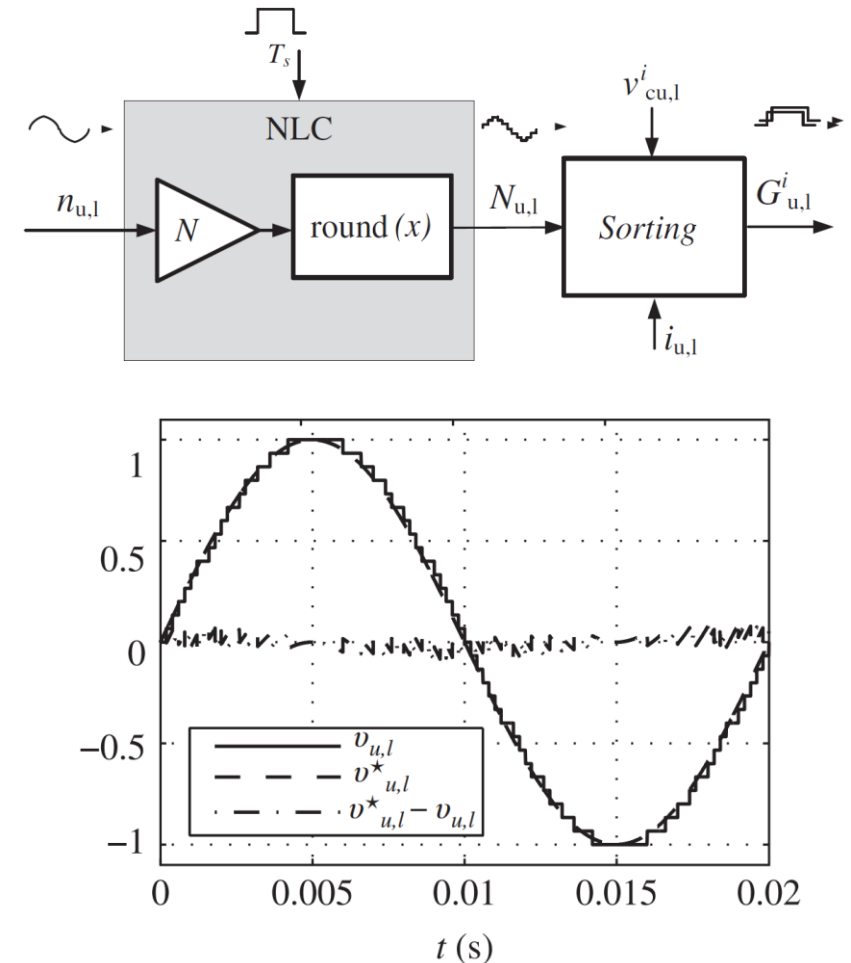


Source: Sharifabadi, K., Harnefors, L., Nee, H. P., Norrga, S., & Teodorescu, R. (2016). Design, control, and application of modular multilevel converters for HVDC transmission systems. John Wiley & Sons.

# Modular Multilevel Converter


- Energy balance

Multilevel PWM

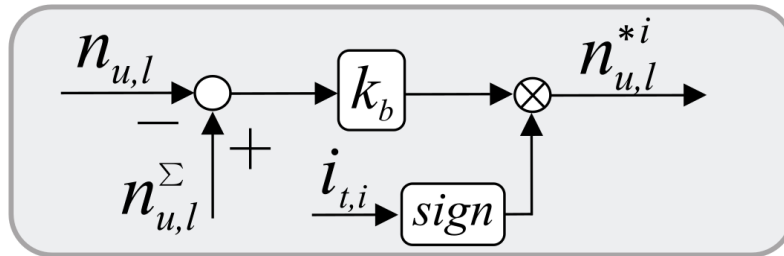

- The modulation index of each cell is modified by a factor that depends on the difference between the voltage of one capacitor with respect to the average voltage of the arm.
- If the current is positive, the modulation index is reduced. If the current is negative, the modulation index is increased.

Nearest-level modulation

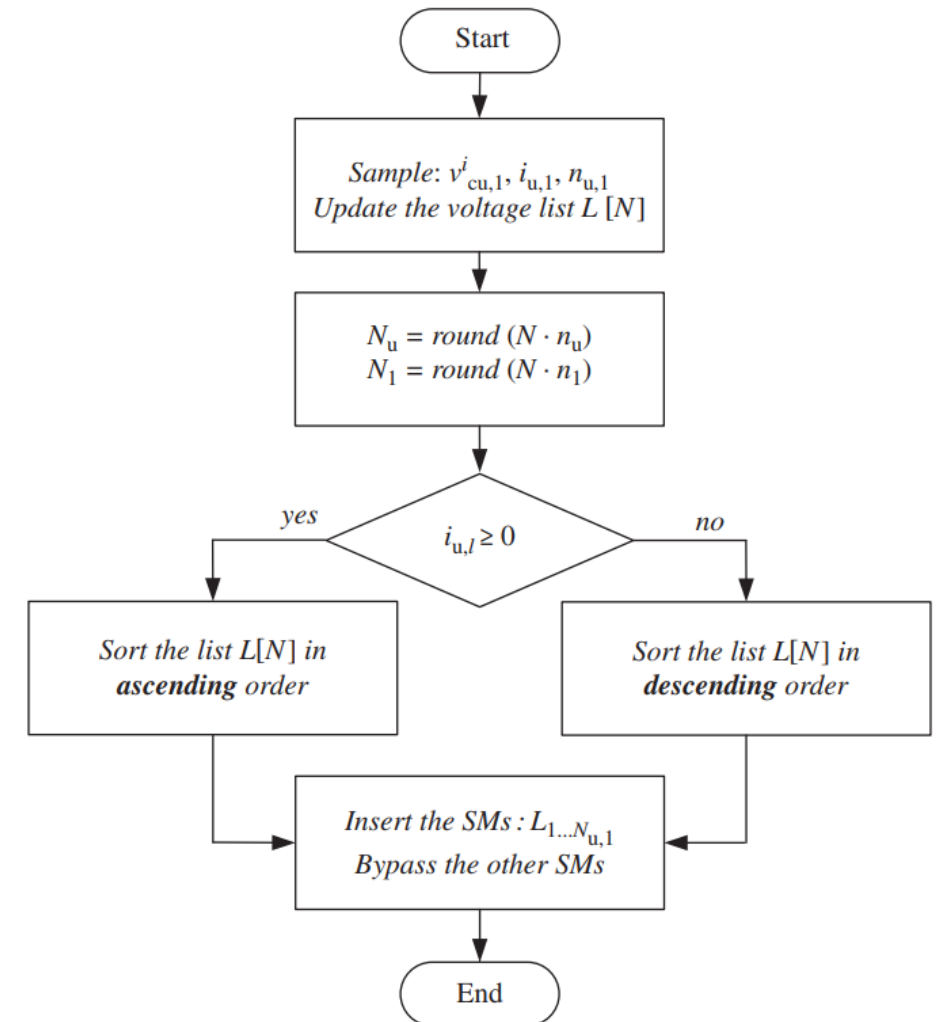

# Outline

---


- Multilevel inverters
- Simulation

# Simulation

- Simulate a three-phase DC/AC converter.

Data:

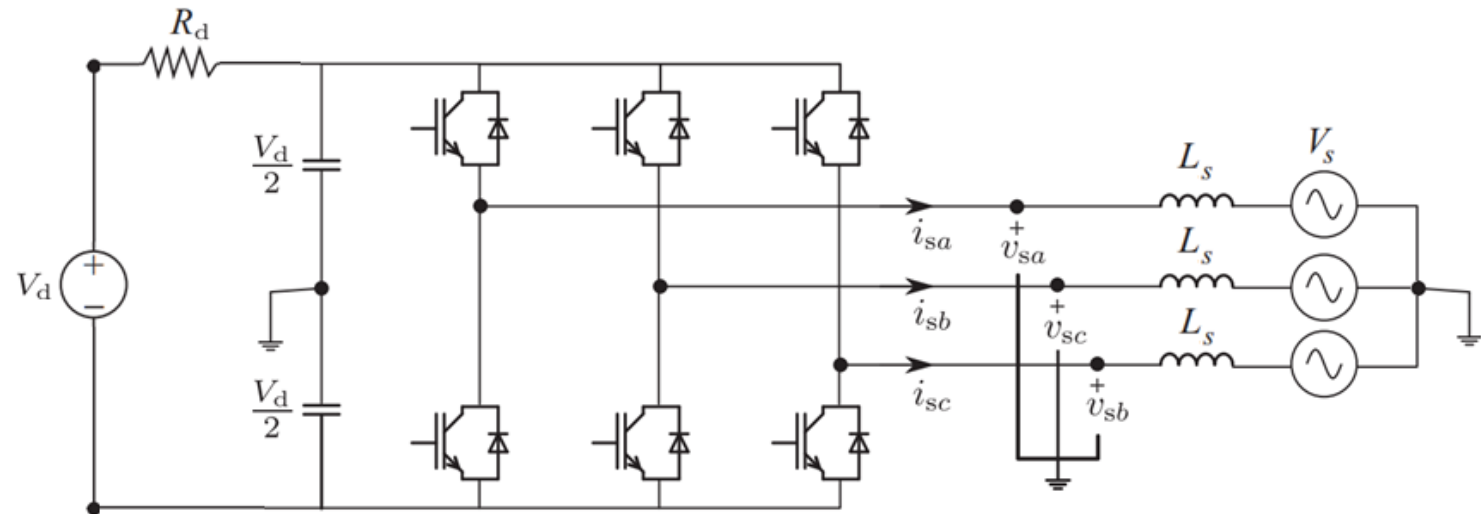- $L_s = 10 \text{ mH}$  ( $R=X/40$ )
- $R_d = 0.1 \text{ Ohm}$
- $V_s = 1200 \text{ V}$  peak phase-to-ground
- $C = 1 \text{ mF}$
- Carrier freq =  $33 \times 50 \text{ Hz}$



- Build the circuit
- Calculate  $V_{dc}$  such that the output voltage at  $M = 0.8$  is equal to  $V_{grid}$ .
- Define the reference amplitude to generate  $900 \text{ V}$  in the output
- Define the angle to export  $200 \text{ kW}$  to the grid
- Define the voltage magnitude to import  $100 \text{ kVAr}$  from the grid

# Electric Energy Conversion

## 8. DC/AC converters – part 2

Vinícius Lacerda  
Electrical Engineering Department  
CITCEA-UPC

