

Electric Energy Conversion

6. DC/DC converters – part 2

Vinícius Lacerda
Electrical Engineering Department
CITCEA-UPC




Outline

- Buck/Boost converters
- Bi-directional converters
- Simulation


Buck/Boost converters

- In some applications it is necessary to generate a DC voltage that can be either **lower** or **greater** than the input. In these cases, we need to use buck/boost converters.
- There are several topologies:
- Both Buck/Boost and Cuk topologies have polarity reversal on the output voltage. The difference between them is that in Cuk, the energy transfer depends on capacitor C1 while in Buck/Boost depends on the inductor.
- The SEPIC has no polarity reversal on the output voltage.

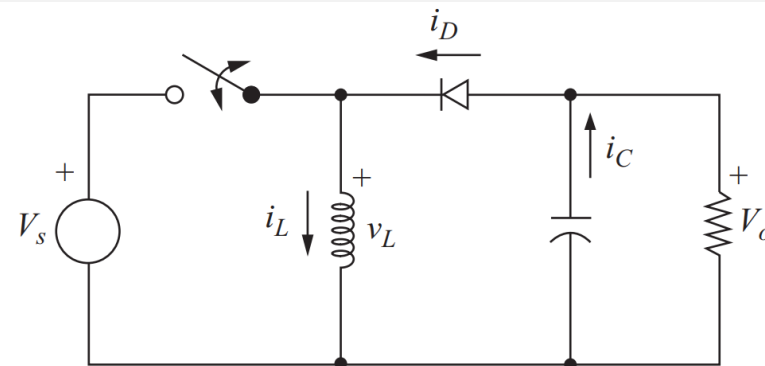


Buck/Boost
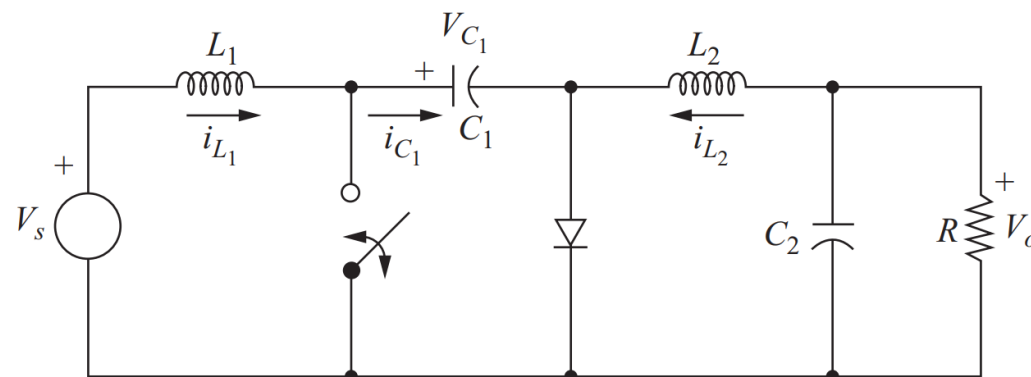
$$V_o = -V_s \left(\frac{D}{1-D} \right)$$



Cuk
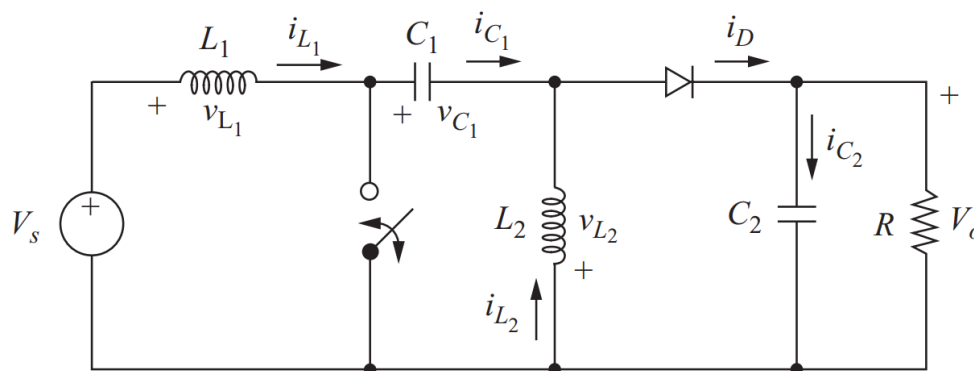
$$V_o = -V_s \left(\frac{D}{1-D} \right)$$




SEPIC

$$V_o = V_s \left(\frac{D}{1-D} \right)$$

SEPIC converter

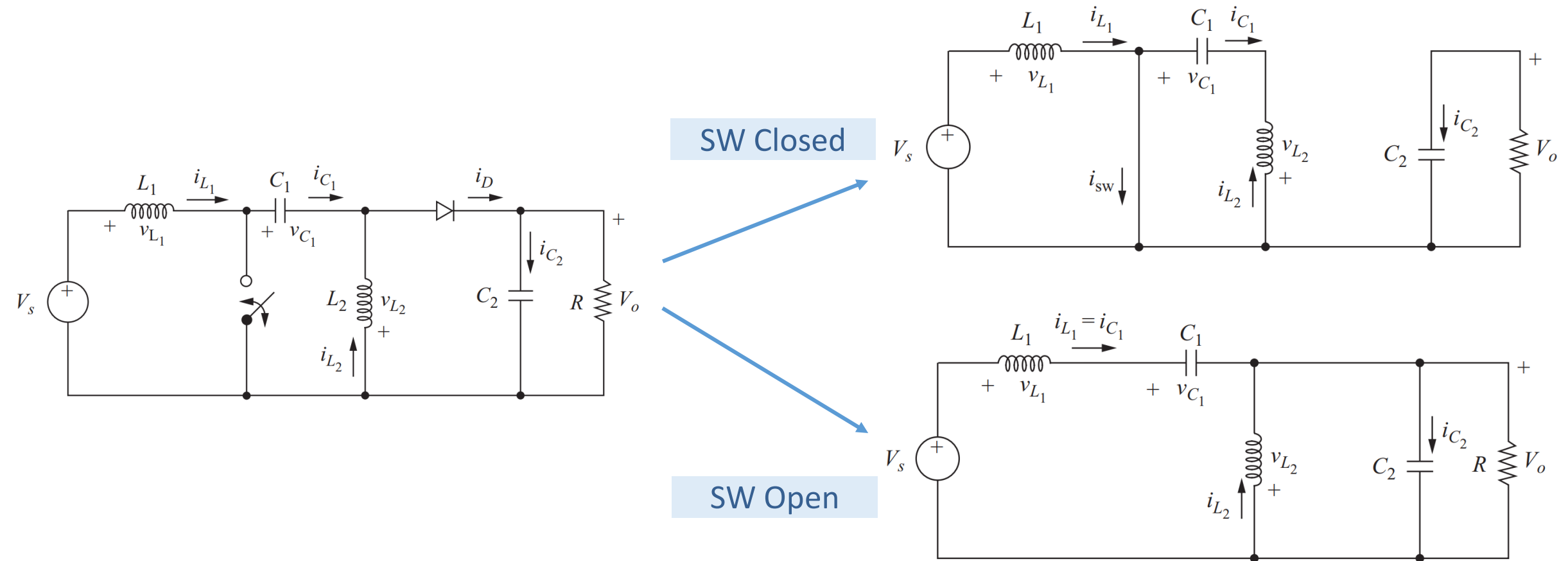- SEPIC means Single-Ended Primary Inductance Converter. It is an interesting topology because its output voltage can be either lower or greater than the input, without polarity reversal.



SEPIC converter

- Let's assume that the inductors and capacitors are big enough to provide continuous operation.
- We will also assume that the inductors and capacitors do not accumulate energy (point of equilibrium).
- Applying KVL around the path containing V_s , L_1 , C_1 and L_2 gives:

$$-V_s + v_{L_1} + v_{C_1} - v_{L_2} = 0 \quad \xrightarrow{\text{Taking the average}} \quad -V_s + 0 + V_{C_1} - 0 = 0 \quad \xrightarrow{\text{Hence}} \quad V_{C_1} = V_s$$

- When the switch is closed (period DT), the diode is OFF and $v_{L_1} = V_s$
- When the switch is open (period $(1 - D)T$), the diode is ON and KVL around the the outer path gives


$$-V_s + v_{L_1} + v_{C_1} + V_o = 0 \quad \xrightarrow{\text{Substituting } V_{C_1} = V_s} \quad -V_s + v_{L_1} + V_s + V_o = 0 \quad \xrightarrow{\text{Hence}} \quad v_{L_1} = -V_o$$

- As the inductor does not accumulate energy:

$$(v_{L_1, \text{ sw closed}})(DT) + (v_{L_1, \text{ sw open}})(1 - D)T = 0$$

$$\downarrow$$
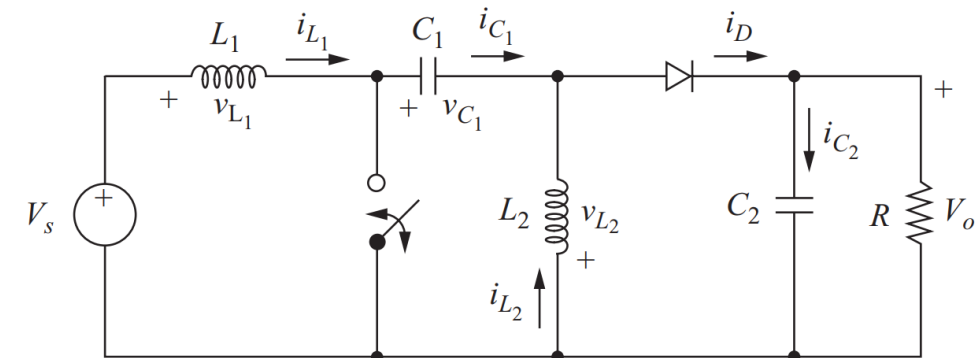
$$V_s(DT) - V_o(1 - D)T = 0 \quad \longrightarrow \quad \boxed{V_o = V_s \left(\frac{D}{1 - D} \right)}$$



SEPIC converter

- To calculate the L_1 current ripples, we can use the conservation of power (neglecting losses):


$$\begin{array}{c}
 P_s = P_o \\
 \downarrow \quad \searrow \\
 P_s = V_s I_s = V_s I_{L1} \quad P_o = V_o I_o
 \end{array}
 \xrightarrow{\text{Hence}} V_s I_{L1} = V_o I_o \xrightarrow{\quad} I_{L1} = I_s = \frac{V_o I_o}{V_s} \quad (\text{average value})$$

- Now, as we know that when the switch is closed $v_{L1} = V_s$

$$v_{L1} = V_s = L_1 \left(\frac{di_{L1}}{dt} \right) = L_1 \left(\frac{\Delta i_{L1}}{\Delta t} \right) = L_1 \left(\frac{\Delta i_{L1}}{DT} \right) \xrightarrow{\text{Hence}} \Delta i_{L1} = \frac{V_s DT}{L_1} = \frac{V_s D}{L_1 f} \quad (\text{ripple})$$

- A similar analysis can be done for L_2 , using KCL, resulting in:
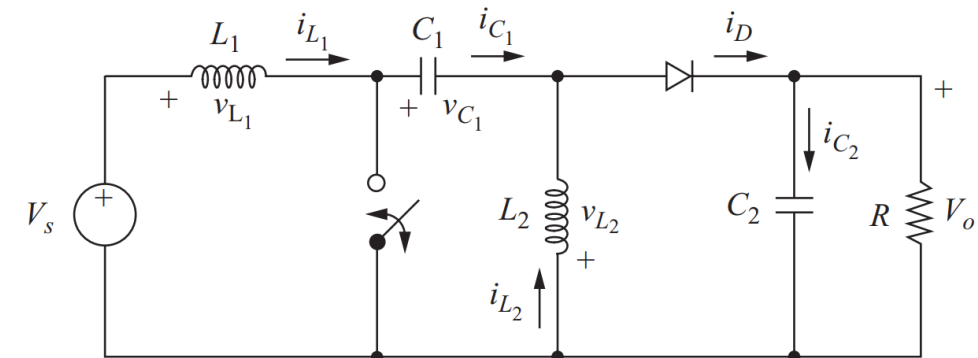
$$\begin{array}{l}
 I_{L2} = I_o \\
 (\text{average value})
 \end{array}
 \quad
 \Delta i_{L2} = \frac{V_s DT}{L_2} = \frac{V_s D}{L_2 f} \quad (\text{ripple})$$




SEPIC converter

- To calculate the C_2 voltage ripple we can use the fact that the output stage composed of a diode, capacitor and load is exactly the same as a Boost converter, so the same relations apply for C_2 .

$$\Delta V_o = \Delta V_{C_2} = \frac{V_o D}{RC_2 f} \longrightarrow C_2 = \frac{D}{R(\Delta V_o / V_o) f}$$

- To calculate the C_1 voltage ripple we use the same steps as done before, deriving the ripple from its charge:

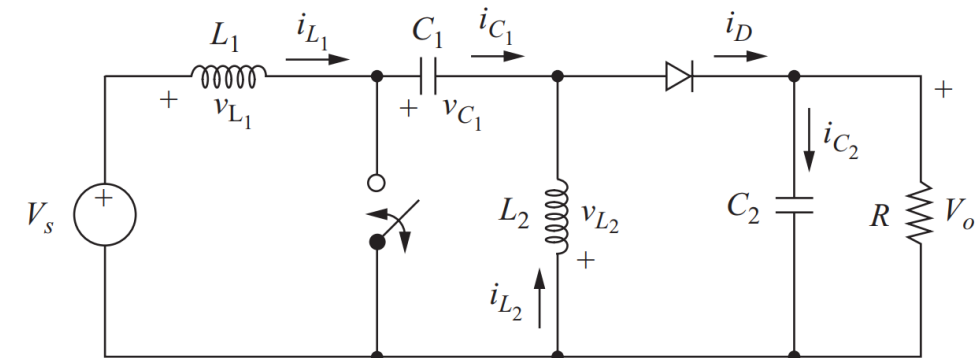
$$\Delta V_{C_1} = \frac{V_o D}{RC_1 f} \longrightarrow C_1 = \frac{D}{R(\Delta V_{C_1} / V_o) f}$$



SEPIC converter - Exercise

- For the SEPIC converter below, determine (consider ideal components):

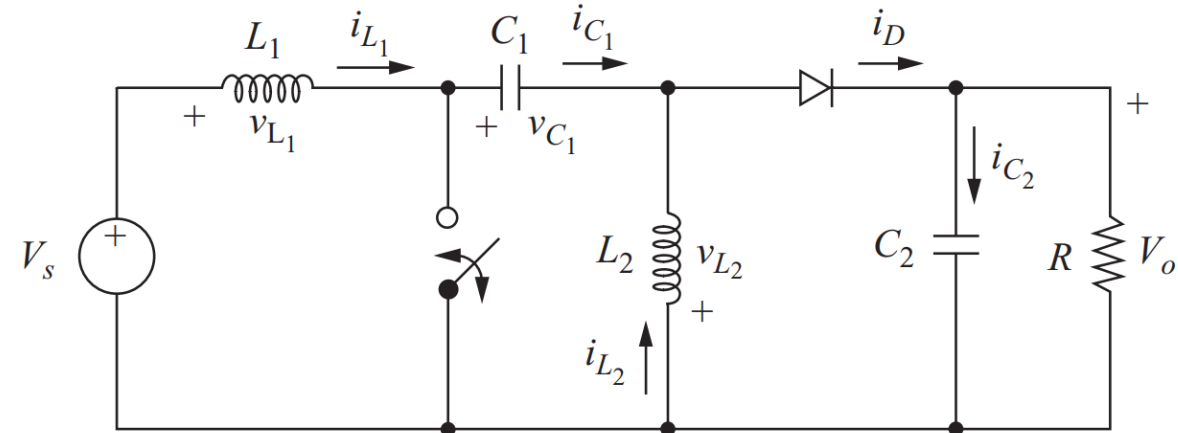- output voltage
- average, maximum and minimum inductor currents
- voltage ripple across each capacitor.



- Data

$$V_s = 9 \text{ V}$$

$$D = 0.4$$

$$f = 100 \text{ kHz}$$

$$L_1 = L_2 = 90 \text{ } \mu\text{H}$$

$$C_1 = C_2 = 80 \text{ } \mu\text{F}$$

$$I_o = 2 \text{ A}$$

- Key equations

$$V_o = V_s \left(\frac{D}{1-D} \right) \quad I_{L1} = \frac{V_o I_o}{V_s} \quad \Delta i_{L1} = \frac{V_s D}{L_1 f} \quad \Delta V_{C2} = \frac{V_o D}{RC_2 f}$$

$$I_{L2} = I_o \quad \Delta i_{L2} = \frac{V_s D}{L_2 f} \quad \Delta V_{C1} = \frac{V_o D}{RC_1 f}$$

SEPIC converter - Exercise

- Solution

$$V_o = V_s \left(\frac{D}{1-D} \right) = 9 \left(\frac{0.4}{1-0.4} \right) = 6 \text{ V}$$

$$I_{L1} = \frac{V_o I_o}{V_s} = \frac{6(2)}{9} = 1.33 \text{ A}$$

$$\Delta i_{L1} = \frac{V_s D}{L_1 f} = \frac{9(0.4)}{90(10)^{-6}(100,000)} = 0.4 \text{ A}$$

Maximum and minimum currents in L_1 are then

$$I_{L1,\max} = I_{L1} + \frac{\Delta i_{L1}}{2} = 1.33 + \frac{0.4}{2} = 1.53 \text{ A}$$

$$I_{L1,\min} = I_{L1} - \frac{\Delta i_{L1}}{2} = 1.33 - \frac{0.4}{2} = 1.13 \text{ A}$$

For the current in L_2 , the average is the same as the output current $I_o = 2 \text{ A}$. The variation in I_{L2} is determined from

$$\Delta i_{L2} = \frac{V_s D}{L_2 f} = \frac{9(0.4)}{90(10)^{-6}(100,000)} = 0.4 \text{ A}$$

resulting in maximum and minimum current magnitudes of

$$I_{L2,\max} = 2 + \frac{0.4}{2} = 2.2 \text{ A}$$

$$I_{L2,\min} = 2 - \frac{0.4}{2} = 1.8 \text{ A}$$

Using an equivalent load resistance of $6 \text{ V} / 2 \text{ A} = 3 \Omega$, the ripple voltages in the capacitors are determined from

$$\Delta V_o = \Delta V_{C2} = \frac{V_o D}{RC_2 f} = \frac{6(0.4)}{(3)80(10)^{-6}(100,000)} = 0.1 \text{ V}$$


$$\Delta V_{C1} = \frac{V_o D}{RC_1 f} = \frac{6(0.4)}{(3)80(10)^{-6}(100,000)} = 0.1 \text{ V}$$

Outline

- Buck/Boost converters
- **Bi-directional converters**
- Simulation

Bi-directional DC/DC converters

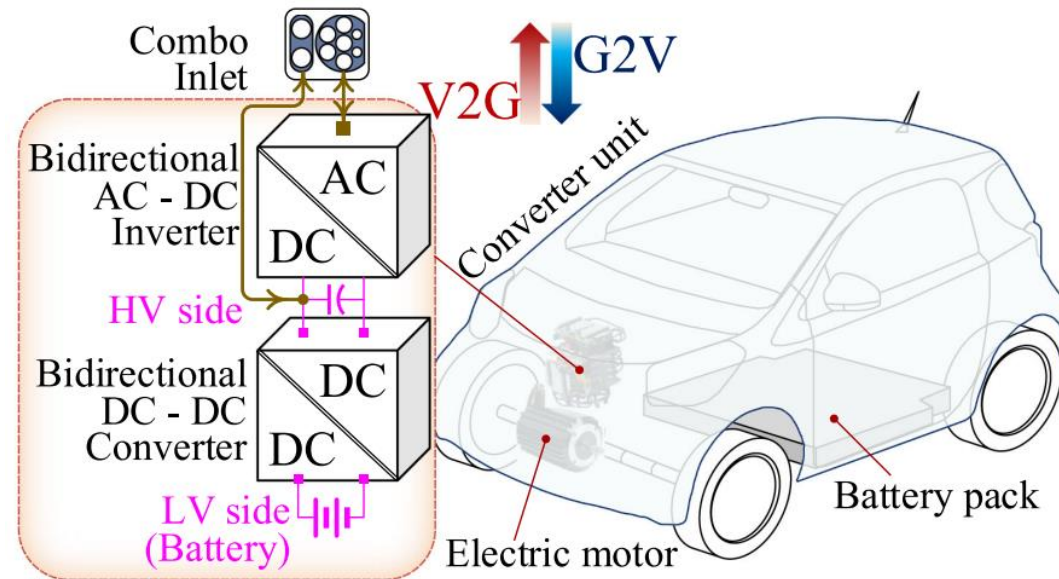
- In some industrial applications, it is required to exchange DC power in two directions.
- In these cases, the DC/DC converter must be **bidirectional** (the current can be reversed).
- This is common in **V2G** applications and **energy storage** applications.



Layout of an EV electrical system.

Bi-directional DC/DC converters

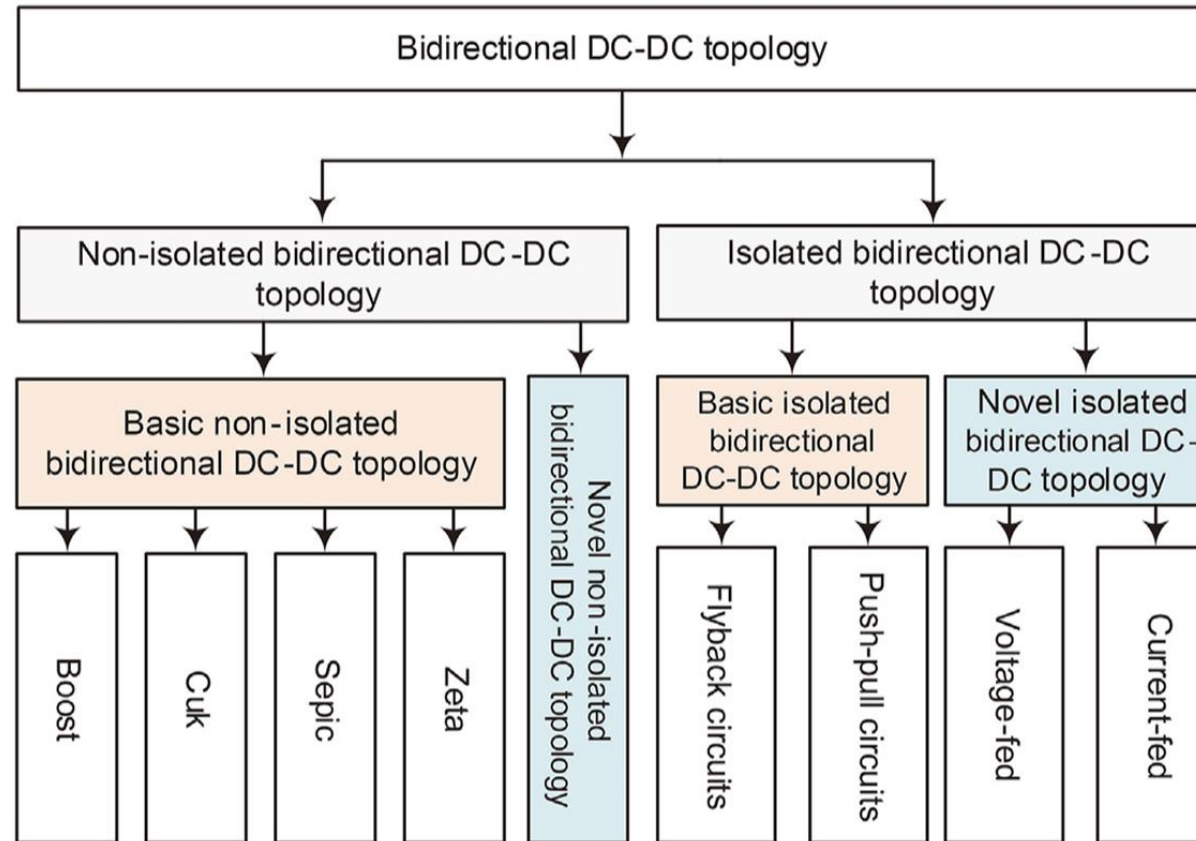- There are many topologies of DC/DC converters. Most of them replace diodes with transistors to allow current flow in both directions.




Source: J. Wang, B. Wang, L. Zhang, J. Wang, N. I. Shchurov, and B. V. Malozyomov, "Review of bidirectional DC-DC converter topologies for hybrid energy storage system of new energy vehicles," Green Energy and Intelligent Transportation, vol. 1, no. 2, p. 100010, Sep. 2022, doi: 10.1016/j.geits.2022.100010.

Bi-directional Buck converter

- The bi-directional buck converter has the same principle of operation of a buck converter, but uses two switches to allow current flowing in both directions.
- The topology with two switches is known as a **synchronous buck converter**.
- The switches 1 and 2 are complementary: when one is ON, the other is OFF, and vice versa.
- The switches can be MOSFETs in low-power applications or IGBTs in medium/high-power applications.


$$V_o = V_s D$$

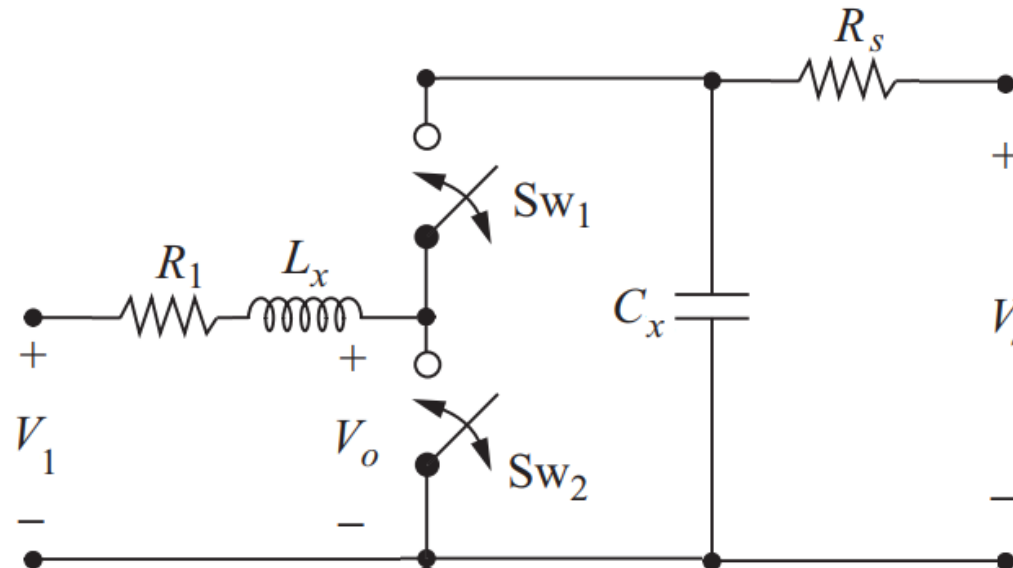The direction of the current will be defined by the difference between V_1 and V_o




Bi-directional Buck converter

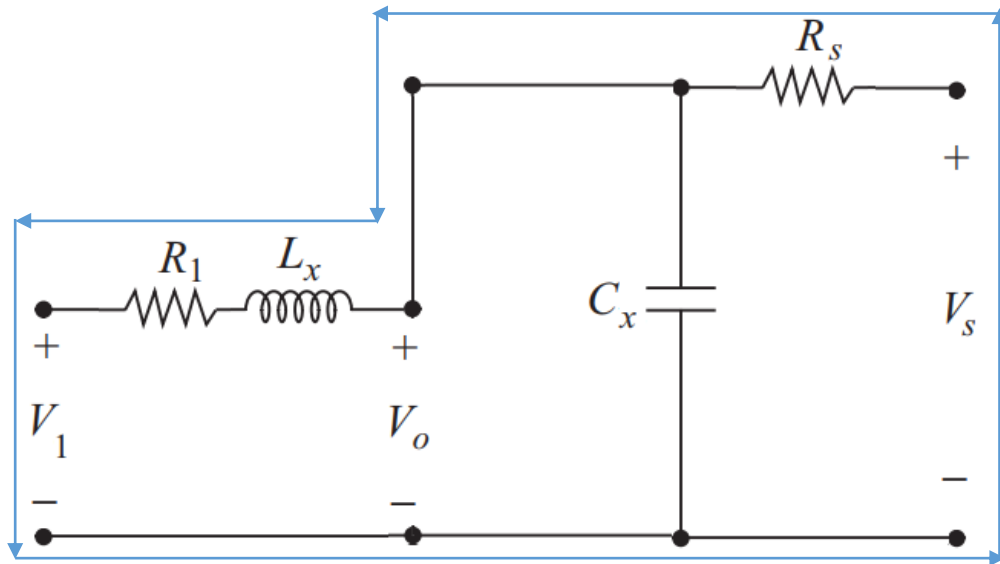
- When SW_1 is closed and SW_2 is open:
- Energy is stored in L_x



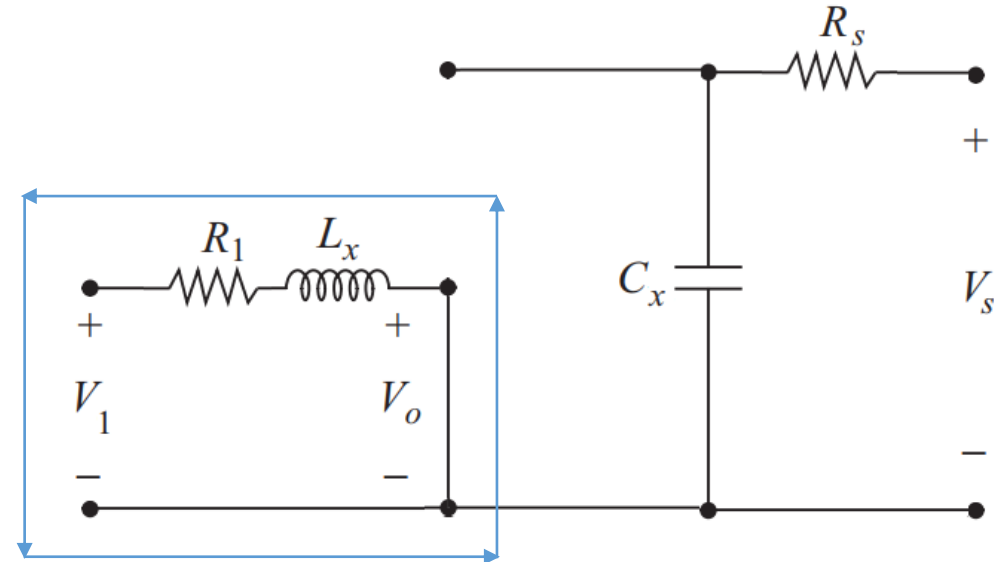- When SW_2 is closed and SW_1 is open:
- Energy is released by L_x



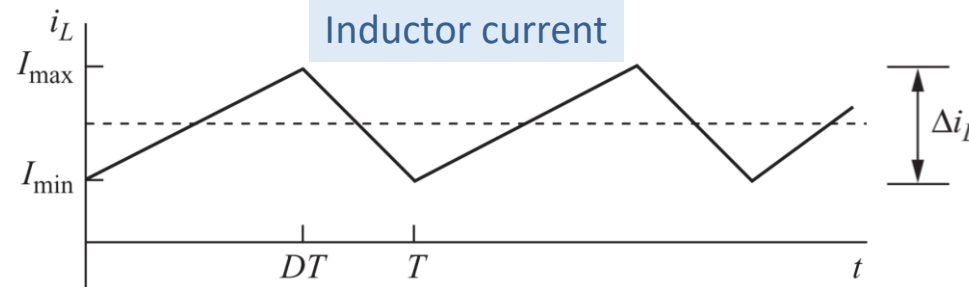If L_x is too big, the current dynamics are slower



- To have continuous current:

$$L = \left(\frac{V_s - V_o}{\Delta i_L f} \right) D = \frac{V_o(1 - D)}{\Delta i_L f}$$

Outline


- Buck/Boost converters
- Bi-directional converters
- **Simulation**

Simulation

- Simulate a bi-directional DC/DC converter.

Data:

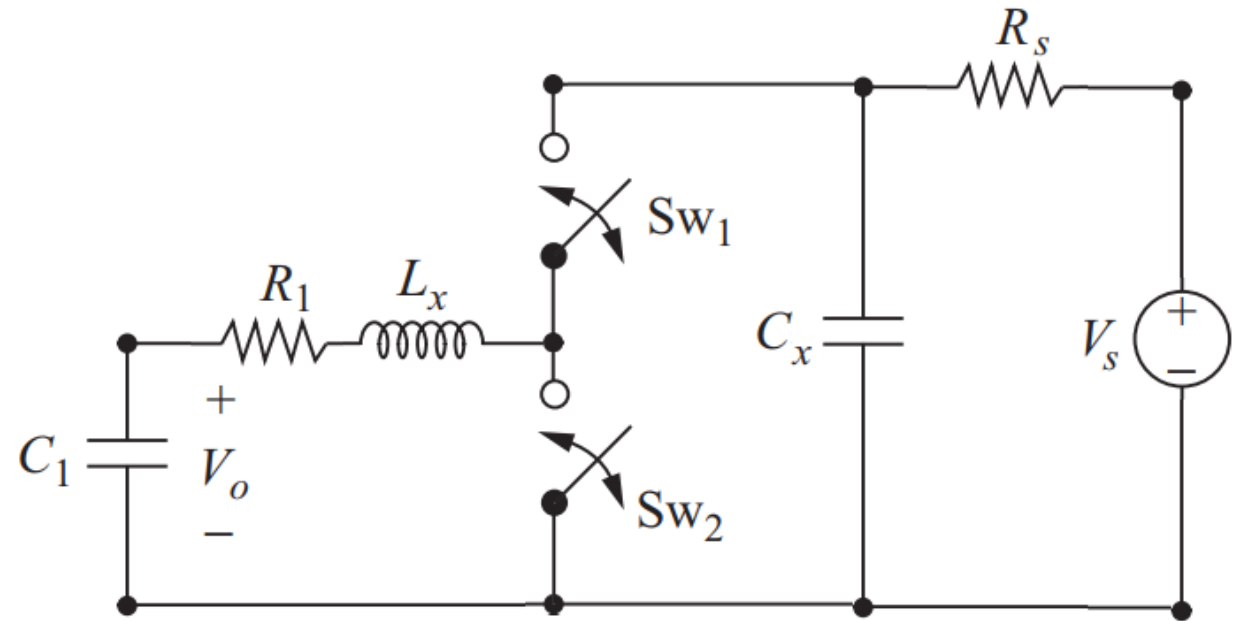- $V_s = 1000 \text{ V (DC)}$ ($R_s = 1 \text{ m}\Omega$)
- $L = 50 \text{ }\mu\text{H}$ ($R_1 = 1 \text{ m}\Omega$)
- $C_x = 50 \text{ }\mu\text{F}$
- $C_1 = 5 \text{ F}$ (initially charged to 500 V)
- $f = 10 \text{ kHz}$
- Start with $D = 0.5$



a) Define $D = 0.8$ and then $D = 0.3$ and plot the power exchanged and C_1 voltage

Electric Energy Conversion

6. DC/DC converters – part 2

Vinícius Lacerda
Electrical Engineering Department
CITCEA-UPC

